

Boolean Algebra, Logic Gates, Circuits

CSIS 2226

What is Boolean Algebra?

- A minor generalization of propositional logic.
 - In general, an *algebra* is any mathematical structure satisfying certain standard algebraic axioms.
 - Such as associative/commutative/transitive laws, *etc.*
 - General theorems that are proved about an algebra then apply to *any* structure satisfying these axioms.
- *Boolean algebra* just generalizes the rules of propositional logic to sets other than **{T,F}**.
 - *E.g.*, to the set **{0,1}** of base-2 digits, or the set **{V_L, V_H}** of low and high voltage levels in a circuit.
- We will see that this algebraic perspective lends itself to the design of *digital logic circuits*.

Claude Shannon's Master's thesis!

Boolean Algebra

- Sections of chapter 11:
 - §1 – Boolean Functions
 - §2 – Representing Boolean Functions
 - §3 – Logic Gates
 - §4 – Minimization of Circuits

§11.1 – Boolean Functions

- Boolean complement, sum, product.
- Boolean expressions and functions.
- Boolean algebra identities.
- Duality.
- Abstract definition of a Boolean algebra.

Complement, Sum, Product

- Correspond to logical NOT, OR, and AND.
- We will denote the two logic values as **0:≡F** and **1:≡T**, instead of **False** and **True**.
 - Using numbers encourages algebraic thinking.
- New, more algebraic-looking notation for the most common Boolean operators:

$\bar{x} \equiv \neg x$ $x \cdot y \equiv x \wedge y$ $x + y \equiv x \vee y$

Precedence order →

Boolean Functions

- Let $B = \{0, 1\}$, the set of Boolean values.
- For all $n \in \mathbb{Z}^+$, any function $f: B^n \rightarrow B$ is called a *Boolean function of degree n*.
- There are 2^{2^n} (wow!) distinct Boolean functions of degree n .
 - B/c $\exists 2^n$ rows in truth table, w. 0 or 1 in each.

Degree	How many	Degree	How many
0	2	4	65,536
1	4	5	4,294,967,296
2	16	6	18,446,744,073,709,551,616.
3	256		

Truth Tables

- A Boolean operator can be completely described using a truth table.
- The truth table for the Boolean operators AND and OR are shown at the right.
- The AND operator is also known as a Boolean product. The OR operator is the Boolean sum.

X AND Y		
X	Y	XY
0	0	0
0	1	0
1	0	0
1	1	1

X OR Y		
X	Y	X+Y
0	0	0
0	1	1
1	0	1
1	1	1

Truth Tables

- The truth table for the Boolean NOT operator is shown at the right.
- The NOT operation is most often designated by an overbar. It is sometimes indicated by a prime mark (') or an "elbow" (^).

NOT X	
X	\bar{X}
0	1
1	0

Boolean Functions

- The truth table for the Boolean function: $F(x, y, z) = x\bar{z} + y$ is shown at the right.
- To make evaluation of the Boolean function easier, the truth table contains extra (shaded) columns to hold evaluations of subparts of the function.

$F(x, y, z) = x\bar{z} + y$					
x	y	z	\bar{z}	$x\bar{z}$	$x\bar{z} + y$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	1

Boolean Functions

- As with common arithmetic, Boolean operations have rules of precedence.
- The NOT operator has highest priority, followed by AND and then OR.
- This is how we chose the (shaded) function subparts in our table.


$F(x, y, z) = x\bar{z} + y$					
x	y	z	\bar{z}	$x\bar{z}$	$x\bar{z} + y$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	1

Boolean Expressions

- Let x_1, \dots, x_n be n different Boolean variables.
 - n may be as large as desired.
- A *Boolean expression* (recursive definition) is a string of one of the following forms:
 - Base cases: $0, 1, x_1, \dots, \text{or } x_n$.
 - Recursive cases: $\overline{E_1}, (E_1E_2), \text{ or } (E_1+E_2)$, where E_1 and E_2 are Boolean expressions.
- A Boolean expression represents a Boolean function.
 - Furthermore, every Boolean function (of a given degree) can be represented by a Boolean expression.

Hypercube Representation

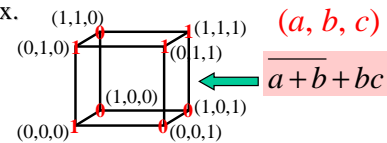- A Boolean function of degree n can be represented by an n -cube (hypercube) with the corresponding function value at each vertex.



Boolean equivalents, operations on Boolean expressions

- Two Boolean expressions e_1 and e_2 that represent the exact *same* function f are called *equivalent*. We write $e_1 \Leftrightarrow e_2$, or just $e_1 = e_2$.
 - Implicitly, the two expressions have the same value for *all* values of the free variables appearing in e_1 and e_2 .
- The operators $\bar{}$, $+$, and \cdot can be extended from operating on expressions to operating on the functions that they represent, in the obvious way.

Boolean functions and digital circuits

- Digital computers contain circuits that implement Boolean functions.
- The simpler that we can make a Boolean function, the smaller the circuit that will result.
 - Simpler circuits are cheaper to build, consume less power, and run faster than complex circuits.
- With this in mind, we always want to reduce our Boolean functions to their simplest form.
- There are a number of Boolean identities that help us to do this.

Some popular Boolean identities

- | | |
|--|--|
| <ul style="list-style-type: none"> Double complement: $\overline{\overline{x}} = x$ Idempotent laws: $x + x = x$, $x \cdot x = x$ Identity laws: $x + 0 = x$, $x \cdot 1 = x$ Domination laws: $x + 1 = 1$, $x \cdot 0 = 0$ Commutative laws: $x + y = y + x$, $x \cdot y = y \cdot x$ | <ul style="list-style-type: none"> Associative laws: $x + (y + z) = (x + y) + z$
$x \cdot (y \cdot z) = (x \cdot y) \cdot z$ Distributive laws: $x + y \cdot z = (x + y) \cdot (x + z)$
$x \cdot (y + z) = x \cdot y + x \cdot z$ De Morgan's laws: $\overline{(x \cdot y)} = \overline{x} + \overline{y}$, $\overline{(x + y)} = \overline{x} \cdot \overline{y}$ Absorption laws: $x + x \cdot y = x$, $x \cdot (x + y) = x$ |
|--|--|
- ← Not true in ordinary algebras.
- also, the Unit Property: $x + \overline{x} = 1$ and Zero Property: $x \cdot \overline{x} = 0$

Simplifying Boolean Functions

- We can use Boolean identities to simplify the function: as follows: $F(X, Y, Z) = (X + Y)(X + \overline{Y})(XZ)$

$(X + Y)(X + \overline{Y})(XZ)$ $(X + Y)(X + \overline{Y})(\overline{XZ})$ $(XX + X\overline{Y} + XY + Y\overline{Y})(\overline{X} + Z)$ $((X + Y\overline{Y}) + X(Y + \overline{Y}))(\overline{X} + Z)$ $((X + 0) + X(1))(\overline{X} + Z)$ $X(\overline{X} + Z)$ $X\overline{X} + XZ$ $0 + XZ$ XZ	Idempotent Law (Rewriting) DeMorgan's Law Distributive Law Commutative & Distributive Laws Inverse Law Idempotent Law Distributive Law Inverse Law Idempotent Law
--	---

Simplifying Boolean Functions

- Sometimes it is more economical to build a circuit using the complement of a function (and complementing its result) than it is to implement the function directly.
- DeMorgan's law provides an easy way of finding the complement of a Boolean function.
- Recall DeMorgan's law states:

$$\overline{(xy)} = \overline{x} + \overline{y} \quad \text{and} \quad \overline{(x+y)} = \overline{x} \cdot \overline{y}$$

Simplifying Boolean Functions

- DeMorgan's law can be extended to any number of variables.
- Replace each variable by its complement and change all ANDs to ORs and all ORs to ANDs.
- Thus, we find the the complement of:

$$F(X, Y, Z) = (XY) + (\overline{XZ}) + (Y\overline{Z})$$
 is:

$$\overline{F(X, Y, Z)} = \overline{(XY) + (\overline{XZ}) + (Y\overline{Z})}$$

$$= \overline{(XY)} \cdot \overline{(\overline{XZ})} \cdot \overline{(Y\overline{Z})}$$

$$= (\overline{X} + \overline{Y})(X + Z)(\overline{Y} + Z)$$

Duality

- The dual e^d of a Boolean expression e representing function f is obtained by exchanging $+$ with \cdot , and 0 with 1 in e .
 - The function represented by e^d is denoted f^d .
- Duality principle:** If $e_1 \Leftrightarrow e_2$ then $e_1^d \Leftrightarrow e_2^d$.
 - Example:** The equivalence $x(x+y) = x$ implies (and is implied by) $x + xy = x$.

Boolean Algebra, in the abstract

- A general *Boolean algebra* is any set B having elements $0, 1$, two binary operators \wedge, \vee , and a unary operator \neg that satisfies the following laws:
 - Identity laws: $x \vee 0 = x, \quad x \wedge 1 = x$
 - Complement laws: $x \vee \neg x = 1, \quad x \wedge \neg x = 0$
 - Associative laws: $(x \vee y) \vee z = x \vee (y \vee z), \quad (x \wedge y) \wedge z = x \wedge (y \wedge z)$
 - Commutative laws: $x \vee y = y \vee x, \quad x \wedge y = y \wedge x$
 - Distributive laws: $x \vee (y \wedge z) = (x \vee y) \wedge (x \vee z),$
 $x \wedge (y \vee z) = (x \wedge y) \vee (x \wedge z).$

Note that B may generally have other elements besides $0, 1$, and we have not fully defined any of the operators!

§11.2 – Representing Boolean Functions

- Sum-of-products Expansions
 - A.k.a. Disjunctive Normal Form (DNF)
- Product-of-sums Expansions
 - A.k.a. Conjunctive Normal Form (CNF)
- Functional Completeness
 - Minimal functionally complete sets of operators.

Sum-of-Products Expansions

- Theorem:** Any Boolean function can be represented as a sum of products of variables and their complements.
 - Proof:** By construction from the function's truth table. For each row that is 1, include a term in the sum that is a product representing the condition that the variables have the values given for that row.

Show an example on the board.

Literals, Minterms, DNF

- A *literal* is a Boolean variable or its complement.
- A *minterm* of Boolean variables x_1, \dots, x_n is a Boolean product of n literals $y_1 \dots y_n$, where y_i is either the literal x_i or its complement \bar{x}_i .
 - Note that at most one minterm can have the value 1.
- The *disjunctive normal form* (DNF) of a degree- n Boolean function f is the unique sum of minterms of the variables x_1, \dots, x_n that represents f .
 - A.k.a. the sum-of-products expansion of f .

Converting

- It is easy to convert a function to sum-of-products form using its truth table.
- We are interested in the values of the variables that make the function true (=1).
- Using the truth table, we list the values of the variables that result in a true function value.
- Each group of variables is then ORed together.

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	$x\bar{z} + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Converting

- The sum-of-products form for our function is:

$$F(x, y, z) = \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}\bar{z} + xy\bar{z} + xyz$$

We note that this function is not in simplest terms. Our aim is only to rewrite our function in canonical sum-of-products form.

x	y	z	$x\bar{z}+y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Conjunctive Normal Form

- A *maxterm* is a sum of literals.
- CNF is a *product-of-maxterms* representation.
- To find the CNF representation for f ,
- take the DNF representation for complement $\neg f$,
 $\neg f = \sum_i \prod_j y_{ij}$
- and then complement both sides & apply DeMorgan's laws to get:
 $f = \prod_i \sum_j \neg y_{ij}$

Can also get CNF more directly, using the 0 rows of the truth table.





Functional Completeness

- Since every Boolean function can be expressed in terms of $\cdot, +, \bar{}$, we say that the set of operators $\{\cdot, +, \bar{}\}$ is *functionally complete*.
- There are smaller sets of operators that are also functionally complete.
 - We can eliminate either \cdot or $+$ using DeMorgan's law.
- NAND \downarrow and NOR \uparrow are also functionally complete, each by itself (as a singleton set).
 - E.g., $\neg x = x \downarrow x$, and $xy = (x \downarrow y) \downarrow (x \downarrow y)$.

§11.3 – Logic Gates


- Inverter, Or, And gate symbols.
- Multi-input gates.
- Logic circuits and examples.
- Adders, "half," "full," and n -bit.

Logic Gate Symbols

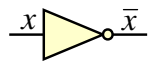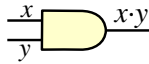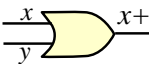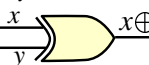- Inverter (logical NOT, Boolean complement). 
- AND gate (Boolean product). 
- OR gate (Boolean sum). 
- XOR gate (exclusive-OR, sum mod 2). 


Multi-input AND, OR, XOR

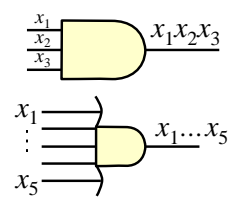- Can extend these gates to arbitrarily many inputs.
- Two commonly seen drawing styles:
 - Note that the second style keeps the gate icon relatively small.




NAND, NOR, XNOR

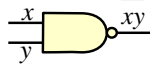- Just like the earlier icons, but with a small circle on the gate's output.




- Denotes that output is complemented.

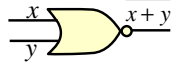


- The circles can also be placed on inputs.

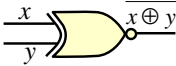- Means, input is complemented before being used.



Buffer

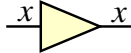- What about an inverter symbol *without* a circle? 
- This is called a *buffer*. It is the identity function.
- It serves no logical purpose, but...
- It represents an explicit delay in the circuit.
 - This is sometimes useful for timing purposes.
- All gates, when physically implemented, incur a non-zero delay between when their inputs are seen and when their outputs are ready.

Combinational Logic Circuits

- **Note:** The correct word to use here is “combinational,” NOT “combinatorial!”
 - Many sloppy authors get this wrong.
- These are circuits composed of Boolean gates whose outputs depend only on their most recent inputs, not on earlier inputs.
 - Thus these circuits have no useful memory.
 - Their state persists while the inputs are constant, but is irreversibly lost when the input signals change.

Combinational Circuit Examples

- Draw a few examples on the board:
 - Majority voting circuit.
 - XOR using OR / AND / NOT.
 - 3-input XOR using OR / AND / NOT.
- Also, show some binary adders:
 - Half adder using OR/AND/NOT.
 - Full adder from half-adders.
 - Ripple-carry adders.

§11.4 – Minimizing Circuits

- Karnaugh Maps
- *Don't care* conditions
- The Quine-McCluskey Method

Goals of Circuit Minimization

- (1) Minimize the number of primitive Boolean logic gates needed to implement the circuit.
 - Ultimately, this also roughly minimizes the number of transistors, the chip area, and the cost.
 - Also roughly minimizes the energy expenditure
 - among traditional irreversible circuits.
 - This will be our focus.
- (2) It is also often useful to minimize the number of combinational *stages* or logical *depth* of the circuit.
 - This roughly minimizes the *delay* or *latency* through the circuit, the time between input and output.

Minimizing DNF Expressions

- Using DNF (or CNF) guarantees there is always *some* circuit that implements any desired Boolean function.
 - However, it may be far larger than needed!
- We would like to find the *smallest* sum-of-products expression that yields a given function.
 - This will yield a fairly small circuit.
 - However, circuits of other forms (not CNF or DNF) might be even smaller for complex functions.